

CMPT220 Midterm Examination
March 12, 2002
Closed Book, 1 Letter Size sheet of notes allowed
Answer all questions on this examination paper
75 MARKS

51

1. (4 marks) When implementing logic functions using CMOS technology, what is the purpose of the pull-up network? The pull-down network?

The pull-up network must be able to attain V_{DD} when necessary and the pull-down network must be the opposite of the pull-up network and must get V_0 when necessary.
 The PUN is also made up of PMOS transistors while the PDN is made up of NMOS transistors.

2. (4 marks) What is the major problem associated with rapidly performing addition or subtraction with larger numbers? What was the solution?

The problem is the loss of precision in the lower-end bits.

3. (4 marks) What is "high-impedance" and why is it important?

High-impedance is a state in a wire usually represented as Z and it is important because it doesn't matter if the output is a 1 or a 0 and it helps solve the fan-out problem.

4. (4 marks) What are two uses for a multiplexer?




One use is to determine which inputs should go on in a circuit depending on what the control signals are set at.
 Another use is to determine what value to return from a look-up table.

5. (10 marks) Given the following table of inputs versus outputs for a logic circuit, answer the following questions using variables of the form IN_x and OUT_x to denote the x^{th} bit and where $x = 0$ represents the lowest order bit.

Input	0	1	3	2	6	7	5	4
Output	0	1	2	4	4	2	1	0

- a) Draw the Karnaugh Maps for each output bit, clearly identifying the inputs and outputs.
b) Minimize each K-Map using SOP form and clearly identify your solution. **Please do not attempt to optimize your solution beyond the K-Map derivation!**

IN_2	IN_1	IN_0	OUT_2	OUT_1	OUT_0
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	0	0	0
1	0	1	0	0	1
1	1	0	1	0	0
1	1	1	0	1	0

   

b) $OUT_2 = IN_1 \overline{IN_0}$

$OUT_1 = IN_1 IN_0$

$OUT_0 = \overline{IN_1} IN_0$

10

6. (10 marks) Write the Entity and Architecture VHDL code for the logic function
 $F(x_2, x_1, x_0) = \Sigma m(1, 2, 4, 7)$

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.all;
```

```
ENTITY testquestion IS
```

```
    PORT (x2, x1, x0 : IN BIT;  
          F           : OUT BIT);
```

```
END testquestion
```

```
ARCHITECTURE LogicFunc OF testquestion IS
```

```
BEGIN
```

```
    F <= (x2 AND NOT x1) AND NOT x0 OR (NOT x2 AND NOT x1 AND x0) OR  
         (x2 AND x1 AND x0) OR (NOT x2 AND x1 AND NOT x0);
```

```
END LogicFunc;
```

7. (8 marks) Express the following K-maps as logic functions of the required form.

a) $F(x_4, x_3, x_2, x_1) = \overline{x_3}\overline{x_2}\overline{x_1} + x_4\overline{x_3}\overline{x_1} +$ Sum of Products Form
 $x_3\overline{x_2}x_1 + x_4x_3x_1 + \overline{x_4}x_3x_2\overline{x_1}$

F

		x ₂ x ₁			
		00	01	11	10
x ₄ x ₃ \	00	1	0	0	0
	01	0	1	0	1
	11	0	1	1	0
	10	1	0	0	1

b) $G(x_1, x_2, x_3, x_4) = (x_2 + x_4)(x_1 + \overline{x_3})(\overline{x_2} + \overline{x_4})$ Product of Sums Form

G

		x ₃ x ₄			
		00	01	11	10
x ₁ x ₂ \	00	0	1	1	0
	01	0	0	0	0
	11	1	0	0	1
	10	0	1	1	0

8. (4 marks) What is the difference between a binary encoder and a binary decoder?


A binary decoder has n inputs and produces 2^n outputs which are one-hot encoded or only one of the outputs is 1. A binary encoder has 2^n inputs which are one-hot encoded and produces n outputs.

9. (8 marks) Given the following VHDL code, draw the timing diagram for the resulting circuit as if you were the Max+plus II development environment.


LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY midterm IS
PORT (w1, w0, s :IN STD_LOGIC;
f :OUT STD_LOGIC);
END midterm;

 ARCHITECTURE behavior OF midterm IS
BEGIN
WITH s SELECT
f <= (w1 AND w0) WHEN '0'
(w1 OR w0) WHEN OTHERS;
END behavior;




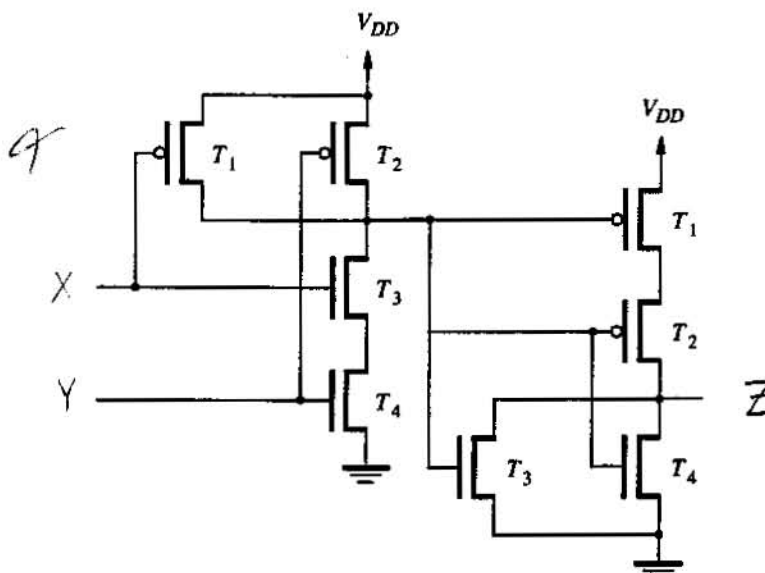10. (4 marks) Express the logic function implemented by the following CMOS circuit in Sum Of Products form.



AND function

x	y	z
0	0	0
0	1	0
1	0	0
1	1	1



 


$$Z = xy$$

11. (9 marks) Analyze the following timing diagram to determine the logic function that it represents. Clearly state the logic function and design a circuit that implements the logic function using NAND gates only.

b1	b0	a1	a0
0	0	1	0
0	1	0	1
1	0	0	1
1	1	1	1

XNOR OR
a1 = EXCLUSIVE NOR
a0 = OR

   

3

12. (6 marks) What is the distinguishing characteristic for each of combinational, sequential, and synchronous systems.

A sequential system is a system where one thing is done and the next thing starts as soon as the first thing finishes.

A combinational system is one where some parts can be done at the same time to speed up the system.

A synchronous system is where everything is done at the same time.